

Unit 2: Circuits

Lecture 1


Electrostatic potential Energy

① $\xrightarrow{r}$ Point $\therefore$ so $V = \frac{kq}{r}$

if we brought another charge ② to p from ∞ , we need to do work: $W = qV$

$$W = \frac{kq_1 q_2}{r}$$

If we want a 3rd charge:

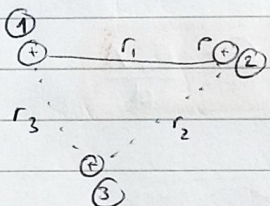

more repulsion = more work

$$W = \frac{kq_1 q_3}{r_3} + \frac{kq_2 q_3}{r_2}$$

So the total system potential energy:


$$U = \frac{kq_1 q_2}{r_1} + \frac{kq_1 q_3}{r_3} + \frac{kq_2 q_3}{r_3}$$

Simplify!

$$U = \frac{1}{2} (q_1 V_1 + q_2 V_2 + q_3 V_3)$$

means POV of 3rd particle.

So find V for other 2.

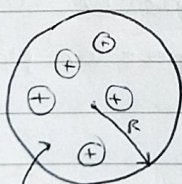

if you load a conductor with charge Q , it acquires a potential V .

$$V = \frac{kQ}{R}$$

dq
from ∞

The work done dU to bring little charge to the conductor is $dU = V dq = \frac{kQ}{R} dq$

$$\text{so } U = \frac{k}{R} \int_0^Q Q dq = \frac{kQ^2}{2R} = \frac{1}{2} QV$$

Capacitance


We know:

$$C = \frac{Q}{V}$$

For spherical conductors:

$$\text{if } V = \frac{kQ}{R} \quad C = \frac{QR}{kQ} = 4\pi \epsilon_0 R^{\leftarrow \text{or}} \left(\frac{R}{k} \right)$$

Parallel Plates (classic capacitor)

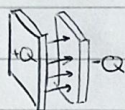


$$E = \frac{Q}{\epsilon_0 A} \quad \text{outside the surface of a conductor}$$

$$V = Ed = \frac{Qd}{\epsilon_0 A} \quad \text{so } C = \frac{\epsilon_0 A}{d}$$

Cylindrical Capacitor

Used in coax cables
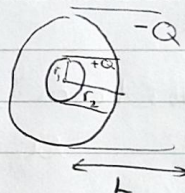
$$C = \frac{2\pi \epsilon_0 L}{\ln\left(\frac{r_2}{r_1}\right)}$$



It takes energy to charge a capacitor. Capacitors store energy as an electric field between the 2 capacitor plates

$$U = \frac{1}{2} QV$$

$$\propto C = Q/V$$

$$\text{so } U = \frac{1}{2} CV^2$$

$$\downarrow \quad \downarrow V = Ed$$

$$U = \frac{1}{2} \frac{\epsilon_0 A}{d} (Ed)^2 =$$

$$\frac{1}{2} \epsilon_0 E^2 \underbrace{Ad}_{\text{volume of space between plates } m^3}$$

energy density $\cdot J m^{-3}$

lecture 2

Example: Cameras!

Energy of 1 flash = 300 Watts $\times$ 3ms = 0.9 J for 100v camera

$$\text{so } U = \frac{1}{2} CV^2 \quad C = \frac{2U}{V^2}$$




$$\text{hence } C = \frac{2 \times 0.9}{100^2} \approx 2 \times 10^{-4} F \quad \text{that's a lot!}$$

How to increase capacitance:

- Increase Area (increases charge) by rolling it up.
- Smaller distance between plates (decrease V)
 - Increases E , so be careful it can't go over 3kV and it discharges.
- Add a dielectric
- Use capacitors in parallel.

Dielectrics

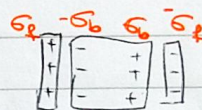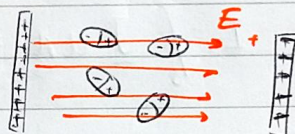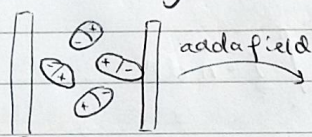non conducting material that can be polarised by an electric field.



They "soak up" or

diminish some electric field,
we can decrease V more!

NO breakdown!

$$E = \frac{E_0}{\kappa} \quad \therefore V = \frac{V_0}{\kappa}$$

$\kappa \leftarrow$ kappa

$$C = \kappa C_0$$

increased capacitance scale factor capacitance it would have sans dielectric


Aire: $E_{\max} = 3 \text{ kV/mm}$

Plexiglas: $E_{\max} = 40$

$\kappa = 3.4$

Batteries

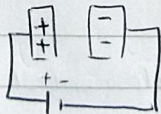Store energy through chemical reactions,
produce a PD between 2 terminals called terminal voltage
charges buildup at plates to diminish PD



In circuits:

in serial

$$C_{eq} = \frac{Q}{V_1 + V_2}$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

in Parallel

$$Q_{\text{total}} = Q_1 + Q_2 = (C_1 + C_2)V$$


$$C_{\text{equivalent}} = C_1 + C_2$$

Current:

Rate of flow of charge:

$$I = \frac{\Delta Q}{\Delta t}$$

$$\text{Ampere} = \text{C s}^{-1}$$

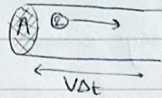

charge density = n

so total charge = qn

total volume = $Av\Delta t$

total charge in volume $\Delta Q = qnAv\Delta t$ *Malcolm*

Hence $I = qnAv$ where in a circuit $I = nAve$ *↖*


Current Density

$$\vec{J} = n v q$$

$$I = \int_S \vec{J} \cdot d\vec{A} = \int_S \vec{J} \cdot \hat{n} dA$$

If J is uniform and the surface is flat:

$$I = J A \cos \theta$$

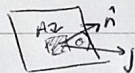


Ohm's law

$$\Delta V = E \Delta L$$


$V = E d$

$$\text{and } R = V / I$$

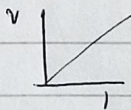

Ohmic

used for resistors

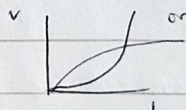

or something else

~~non~~ non-Ohmic

diodes, LEDs, lamps.


Resistivity

$$R = \rho \frac{L}{A} \quad (\rho \text{ is fundamental property})$$

$$\frac{1}{\rho} = \text{conductivity } \sigma \quad \text{units } \Omega^{-1} \text{m}.$$

Lecture 3

Energy in Electric Circuits.

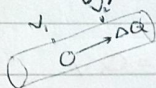

$$\Delta u = \Delta Q (V_2 - V_1) = \Delta Q V$$

overtime Δt :

$$P = \frac{\Delta u}{\Delta t} = \frac{\Delta Q}{\Delta t} V = IV$$

$\Delta Q = I \Delta t$

Power lost due to Joule heating in a resistive conductor

$$P = I^2 R = V^2 / R \quad \leftarrow \text{add } V = IR$$

Joule heating is like electric friction. Friction imposed by atoms in the conductor on the moving charges.

A battery does work on charges by raising the charges through the potential between its terminals. not a force!

Work done per charge = electromotive force $\mathcal{E}$ (in V)


$$P = \frac{\Delta Q \mathcal{E}}{\Delta t} = I \mathcal{E}$$

Real batteries aren't 100% efficient. It uses some of the circuit's energy & it has its own resistance, so:

$$R = r$$

$$V_a - V_b = \mathcal{E} - Ir$$

Terminal (battery) voltage

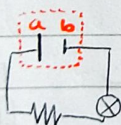

As we increase current, Voltage drops in circuit

In a Simple circuit:

$$V = V_a - V_b = \mathcal{E} - Ir$$

$$V = IR$$


$$\text{so } IR = V_a - V_b = \mathcal{E} - Ir$$

$$\mathcal{E} = I(R + r) \quad \text{in series, so } R_{\text{tot}} = R + r$$

similar to $\frac{V}{R} \rightarrow$

$$I = \frac{\mathcal{E}}{R + r}$$

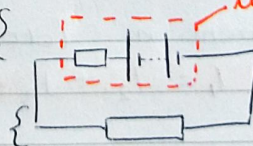line shows mini resistor is just internal resistance.



Energy stored in a battery:


$$E_{\text{stored}} = Q \mathcal{E}$$

↑
charge delivered
over its LIFETIME

Similar to $E = QV$

Behaviour in resistors:

In Series

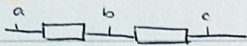


$$V_{\text{total ac}} = V_{ab} + V_{bc}$$

$$V = IR$$

$$V = IR_1 + IR_2$$

In parallel

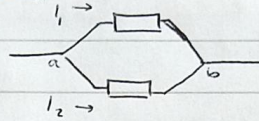

$$I = I_1 + I_2$$


$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = R_1 + R_2$$

Ohmic components


where $V = IR$

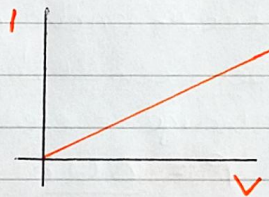

Diodes

$R \sim 0$ above V_c

$R \sim \infty$ below V_c

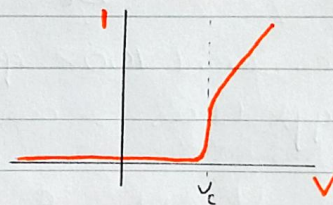

Diodes are good to
make AC!

Kirchhoff's laws


- 1 Sum of all voltages around a closed loop = 0

$$\oint \mathcal{E} \cdot d\mathbf{r} = 0$$




- 2 Total Current in = total current out

$$I_1 = I_2 + I_3$$

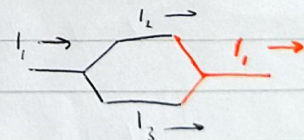


RC Circuits (Resistor Capacitor)

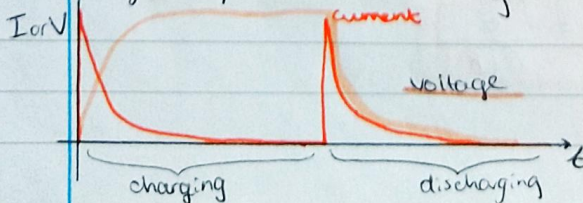charge a capacitor w/ a battery then switch it off to discharge:



For

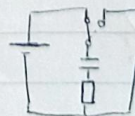

discharging current
can go -ve sometimes,
depends on direction.

Charging & Discharging

Big Voltage between plates.

Big Voltage = Big Current

so large flow of charge.

$$V = \frac{Q}{C} = \frac{dQ}{dt} R$$

-1 ↓

Charge builds up, it

equalises. Smaller charge

= Small Voltage = Small

Force = Small current

Discharging

Exponential

Decrease

in current & voltage when discharging

Discharging Equations

$$\frac{Q}{C} = - \frac{dQ}{dt} R$$

$$\frac{dQ}{dt} = - \frac{Q}{RC} \Rightarrow \frac{dQ}{Q} = - \frac{1}{RC} dt$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = - \frac{1}{RC} \int_0^t dt$$

$$\ln Q/Q_0 = - \frac{t}{RC}$$

$$Q = Q_0 e^{-\frac{t}{RC}}$$

$RC = \tau$ sometimes

Hence:

$$I = I_0 e^{-\frac{t}{RC}}$$

0 Voltage between plates.

Large current since no

force opposing emf.

charge builds up

Voltage increases,

opposes emf, so I decreases.

Charging

Opposite exponential

decrease.

Charging Equations:

$$\mathcal{E} - \frac{dQ}{dt} R - \frac{Q}{C} = 0$$

$$Q = C\mathcal{E}(1 - e^{-\frac{t}{RC}})$$

Hence:

$$I = I_0 e^{-\frac{t}{RC}}$$